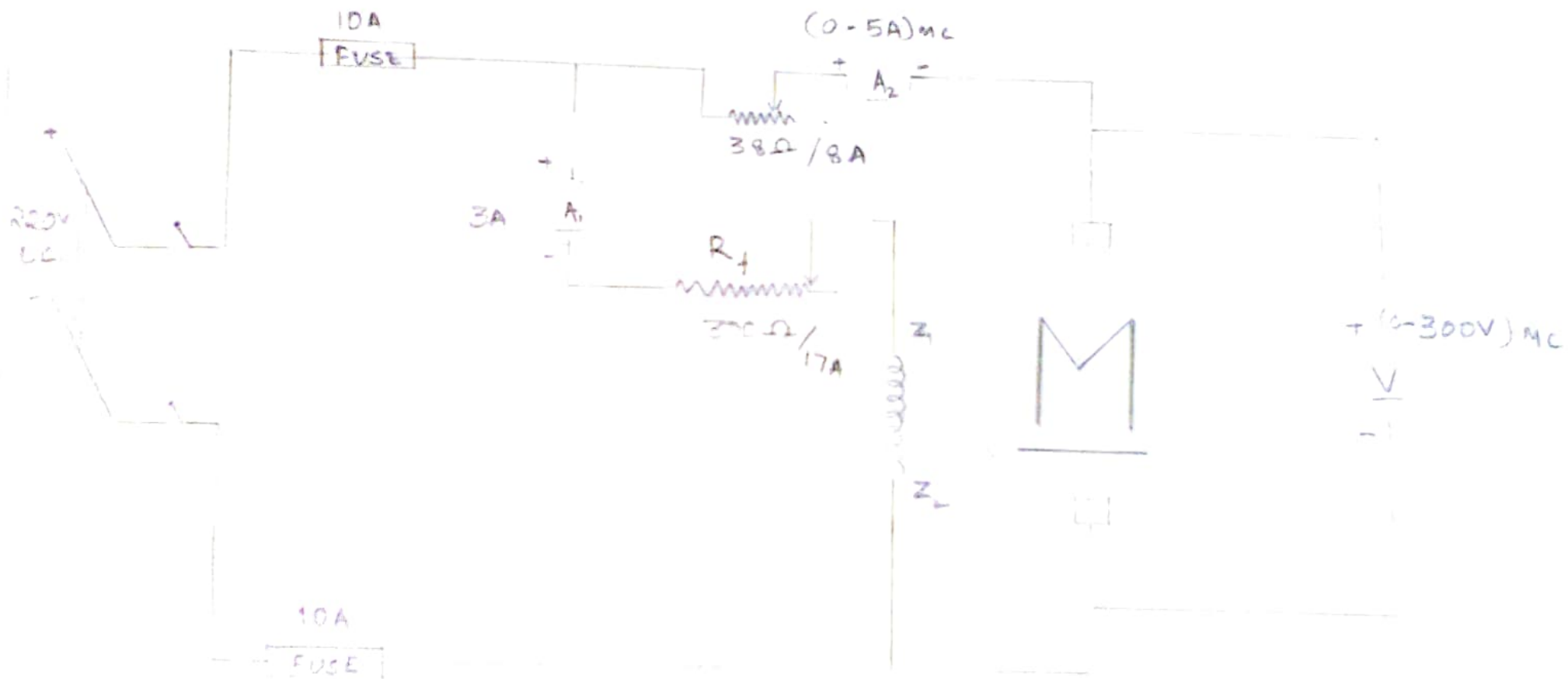


CIRCUIT DIAGRAM



EXPERIMENT NO - 2

AIM OF THE EXPERIMENT

Speed control of DC motor by

- Variation of armature circuit resistance.
- Variation of field circuit resistance.

EQUIPMENTS AND INSTRUMENTS USED:

- A dc shunt motor with starters.
- One moving coil ammeter 0-5 A.
- One moving coil ammeter 0-3 A.
- One moving coil voltmeter 0-300 V.
- One rheostat of 500 ohms 5 Amps.
- One rheostat of 300 ohms, 2 Amps.
- One S.P.S.T Switch.

THEORY:

If V is the applied voltage across the motor terminals, E_b is the back emf developed, then $V = E_b + I_a R_a$, where I_a and R_a are the current and resistance in the armature circuit respectively.

$$\text{But } E_b = \frac{\phi Z N P}{60 A} = k \phi N.$$

$$\text{Hence, } V = k \phi N + I_a R_a$$

$$\text{or } N = \frac{k' (V - I_a R_a)}{\phi}$$

This shows that:-

- 1) An increase in the $I_a R_a$ drop will decrease the value of speed if V remains constant.
- 2) Speed varies inversely as the field flux and hence varies inversely as the exciting current, if below saturation. Thus by increasing the resistance in the armature circuit, a motor can be operated at speeds

CASE A ARMATURE RESISTANCE CONTROL

$$I_f = 1.6 \text{ A} \quad R_a = 11 \Omega$$

ω	V_a (V)	I_a (A)	$E_b = V_a - I_a R_a$ (V)	n (rpm)
1	145	1.57	143.27	952
2	152	1.60	150.24	993
3	158	1.67	156.16	1030
4	165	1.70	163.13	1085
5	172	1.75	170.27	1125
6	182	1.75	180.07	1200
7	196	1.825	193.99	1300

$$I_f = 1.5 \text{ A} \quad R_a = 11 \Omega$$

ω	V_a (V)	I_a (A)	$E_b = V_a - I_a R_a$ (V)	n (rpm)
1	146	1.50	144.35	975
2	154	1.65	152.185	1015
3	160	1.70	158.13	1075
4	166	1.70	164.13	1100
5	173	1.725	171.10	1170
6	183	1.75	180.07	1250
7	186	1.8	184.02	1335

below normal. By increasing the resistance in the field circuit, a motor can be operated at speeds above normal.

PROCEDURE:

Case A: Speed control by variation of armature circuit resistance


- (i) Connect the circuit as in the diagram. Adjust R_a and R_f zero at the time of starting the motor (which is run on no load) with the motor starter.
- (ii) The motor is on no load. Adjust R_a and bring the motor to its rated speed. Note the terminal voltage, V and normal excitation which corresponds to the rated speed of the motor. Keep constant throughout. During starting, ammeter A_a may be bypassed.

Case B: Speed control by variation of field circuit resistance

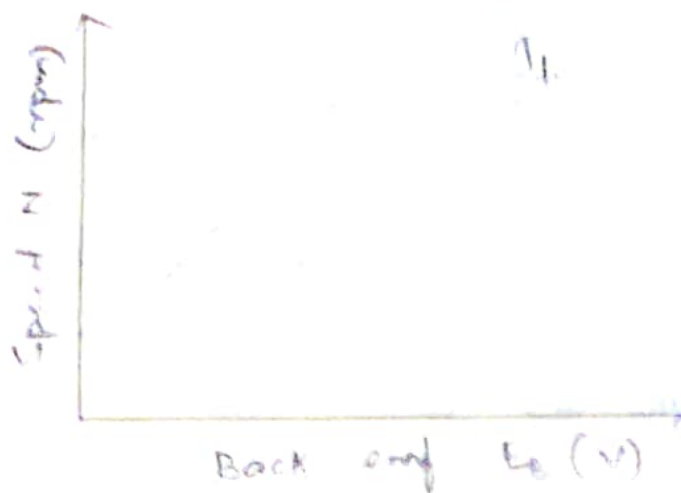
- (i) Run the motor as before and bring it to its rated speed at no load.
- (ii) Cut out the field regulating resistance, R_f in steps and note the speed and the field current, I_f in each case. Keep the voltage across the armature constant. Take readings for decreasing values of speed by increasing field current.
- (iii) Take values of readings for increasing values of speed corresponding to same values of I_f as in (ii).
- (iv) Measure R_f after test.

MODEL GRAPH

$E_b \propto V_b N$ - Armature resistance control



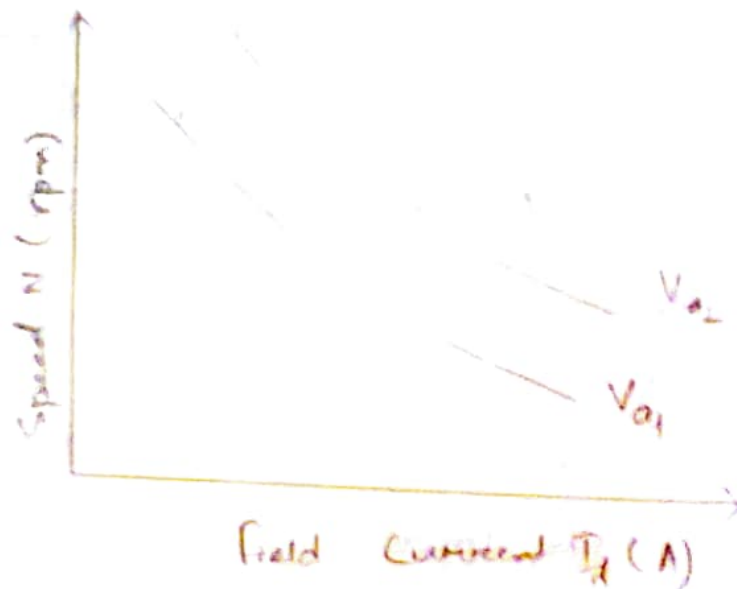If $V_b N/k_a$ const: (Field resistance control)



MACHINE DETAILS

PARAMETER	RANGE
VOLTAGE	220V
RATED SPEED	1200 rpm
CURRENT	30A
WINDING	Combined

FORMULA USED :

$$E_b = V_b - I_a R_a$$

Where

E_b = Back emf

I_a = current flowing through armature

R_a = Armature resistance

DISCUSSION :

Case A : Armature Resistance Control.

Advantage :

- i) Since I_a is constant, torque is constant.
- ii) Speed can be varied from '0' to the rated speed.
- iii) Economical for short time duty.

Disadvantage :

- i) Poor speed regulation. Because of manual work in varying the external resistance, the accuracy is less.
- ii) Lower efficiency & higher running cost due to high external resistance copper loss.

Case B

Advantage :

- i) Speed can be varied above rated speed.
- ii) Output is constant.
- iii) Efficiency is good.

Disadvantage :

At high speed I_f (field current) is small, hence due to high I_a there is a huge amount of sparking.

Case B - Field Resistance Control (V_a constant)

$V_a = 150V$

I_a	I_f (A)	Speed (rpm) with decreasing I_f
1	1.75	948
2	1.60	988
3	1.50	1004
4	1.40	1030
5	1.30	1050
6	1.20	1086
7	1.10	1120
8	1.00	1160
9	0.90	1206

$V_a = 170V$

I_a	I_f (A)	Speed (rpm) with increasing I_f
1	0.90	1408
2	1.00	1366
3	1.10	1314
4	1.20	1272
5	1.30	1226
6	1.40	1180
7	1.50	1146
8	1.60	1118
9	1.70	1100

Handwritten signature and date 22/11/22